

## Summer2018 CSE 140L Lab 1 Assignment – UCSD Alarm Clock

August 2018


# Clock Behavioral Diagram

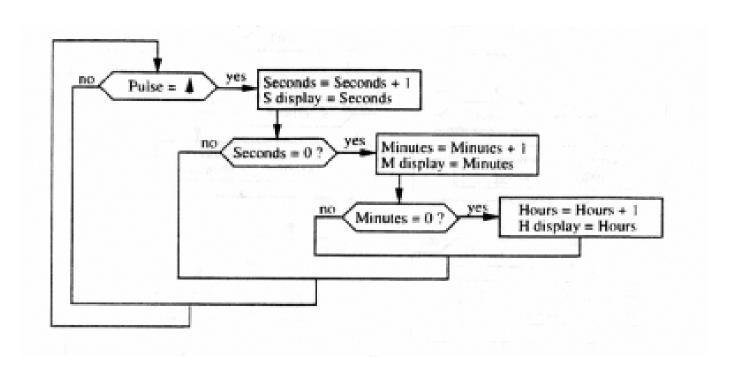


# Alarm Behavioral Diagram

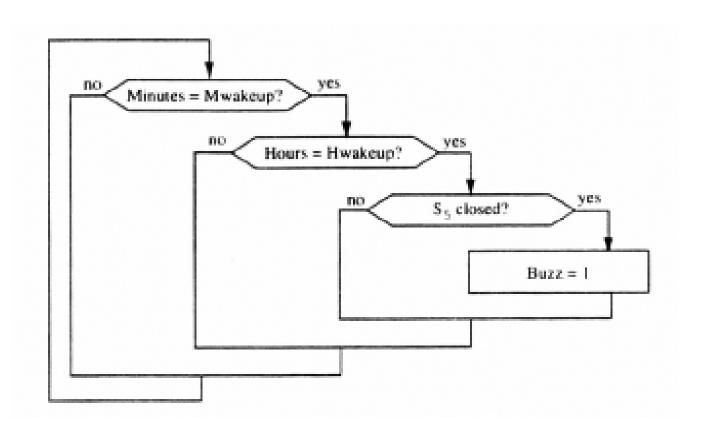

# Combined Behavioral Diagram

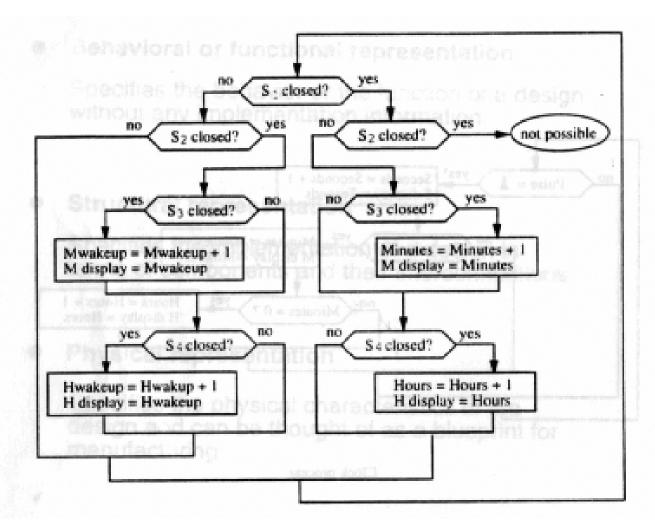

# Structural Diagram

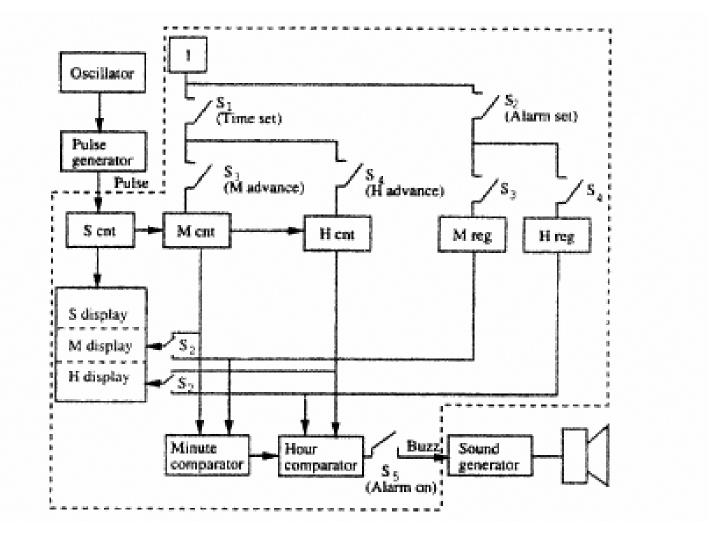

## **Behavioral Description**

### Part 1: Basic alarm clock

- User can adjust the clock time and the alarm time.
- A single set of LCDs that display:
  - The alarm time when the user is setting the alarm;
  - The current time in all other cases.
- User can turn the alarm on or off.
- If the alarm is on, the buzzer goes high when
  - clock hour = alarm hour, and
  - clock minutes = alarm minutes.

## **Behavioral Description**

- Part 1: Basic alarm clock
- Part 2: Days and Months
  - The alarm clock keeps track of the day of week, day of month, and month of year information, and displays it on 7-seg Disp I/O
  - Requires 6 new counters
    - DayOfWeek, DayOfMonth, MonthOfYear for current time
    - DayOfWeek, DayOfMonth, MonthOfYear for alarm time
  - Should be displayed in the same manner as in Part 1, where:
    - The alarm date is displayed when setting the alarm
    - The current date is displayed otherwise

## Components Provided for Part 1

#### ClockDev:

Seconds are incremented at each CLK cycle as in a regular clock. When
its Set input is set, clock time can be adjusted by incrementing hours and
minutes using SM (Set Minute) and SH (Set Hour) inputs.

#### AlarmDev:

 Very similar to ClockDev except that this block has neither a CLK input nor output for seconds.

#### LCD Interface:

 Takes a 6-bit input number (0 to 59) and displays it on 7-segment displays as two decimal digits.

### 6Comp:


6-bit comparator that gives a '1' output if the two inputs are the same.

#### MUX-2x6:

 6-bit 2-to-1 multiplexer that selects one of the two 6-bit inputs and directs it to its output.
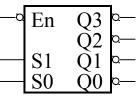
## Decoder-4 (SystemVerilog library component):

- If En == 1, all output = 1;
- If En == 0, For i = 0 to 3, Qi = 0 if S1S0 == i;



# Components to be Implemented for Part 2

### DayOfWeek

- Represents day of week.
- Should use provided Counter-4 for basis of implementation.
- (Current Time) Should count from 1 to 7.
- (Current Time) Can be incremented via SPDT Pushbutton (independently of DayOfMonth) or through rollover of hours (in parallel with DayOfMonth).
- (Alarm Time) Should count from 0 to 7.
- (Alarm Time) Can be independently incremented via SPDT Pushbutton.
- (Alarm Time) If set to 0, then the value is ignored when evaluating logic for the BUZZER.

# Components to be Implemented for Part 2

## DayOfMonth

- Represents day of month
- Should use provided Counter-8 for basis of implementation
- (Current Time) On months 1, 3, 5, 7, 8, 10, and 12, this should count from 1 to 31.
- (Current Time) On months 4, 6, 9, and 11, this should count from 1 to 30.
- (Current Time) On month 3, this should count from 1 to 28.
- (Current Time) Can be incremented via SPDT Pushbutton (independently of DayOfWeek) or through a rollover of the hours (in parallel with DayOfWeek).
- (Alarm Time) Should always count from 0 to 31
- (Alarm Time) Can be independently incremented via SPDT Pushbutton
- (Alarm Time) If set to 0, then the value is ignored when evaluating logic for the BUZZER

# Components to be Implemented for Part 2

#### MonthOfYear

- Represents month of the year
- Should use provided Counter-4 for basis of implementation
- (Current Time) Should count from 1 to 12
- (Current Time) Can be incremented only through rollover of DayOfMonth
- (Alarm Time) Should count from 0 to 12
- (Alarm Time) Can be independently incremented via SPDT Pushbutton
- (Alarm Time) If set to 0, then the value is ignored when evaluating logic for the BUZZER

# Component Increment Rules for Part 2

#### Current Time

- DayOfWeek and DayOfMonth are increment independently when setting the current time.
- DayOfWeek and DayOfMonth are incremented in parallel upon a rollover of the hours.
- MonthOfYear cannot be set directly.
- Ensure always correct date by appropriate rollover.

#### Alarm Time

All counters can be set independently, even to an invalid date.

# Making Custom Components

### To make a custom component:

- 1. Design a circuit that implements the component's functionality
- 2. Identify the component's inputs and outputs, attach ports to your circuit accordingly
  - You must name your ports: right click the port and click "name"
- 3. Open a new file (File → New → Device Symbol)
- 4. Import pin list from existing design
  - Options → Subcircuit and Part Type → Create subcircuit symbol and select open circuit to attach to it
- 5. Draw your circuit
- 6. Place the pins on the circuit (from the left)
  - Click the appropriate buttons for the desired direction of pins
- 7. Save the component in a library of your choice